

MINI-LAB 07

We use Laplace transforms to investigate how (electrical) circuits response to perturbations.

1 Heaviside functions, t -shifting

Definition. The *Heaviside (step) function* $u(t - a)$ is defined as

$$u(t - a) = \begin{cases} 0 & \text{if } t < a \\ 1 & \text{if } t > a \end{cases}. (a \geq 0)$$

The Laplace transform is

$$\mathcal{L}[u(t - a)] = \int_0^\infty e^{-st} u(t - a) dt = \int_a^\infty e^{-st} dt = \left[-\frac{e^{-st}}{s} \right]_{t=a}^{t \rightarrow \infty} = \frac{e^{-as}}{s}$$

Theorem. (*Frequency-shifting*) If $F = \mathcal{L}(f)$, then the frequency-shifted function $F(s - a)$ is the Laplace transform of $\tilde{f}(t) = e^{at} f(t - a)$

$$\mathcal{L}(\tilde{f})(s) = \mathcal{L}(e^{at} f(t - a))(s) = F(s - a).$$

Theorem. (*Time-shifting*) If $F = \mathcal{L}(f)$, then the time-shifted function $\tilde{f}(t) = f(t - a)u(t - a)$ has Laplace transform

$$\mathcal{L}(\tilde{f})(s) = \mathcal{L}(f(t - a)u(t - a))(s) = e^{-as} F(s).$$

2 Circuit response to perturbations

2.1 Switch circuit on over time interval

A perturbation of amplitude V_0 applied for time interval $t \in [a, b]$ (e.g., voltage for electrical circuits) is

$$v(t) = V_0[u(t - a) - u(t - b)].$$

```
In[2]:= v[t_,V0_,a_,b_] := V0 (UnitStep[t-a]-UnitStep[t-b]);
vplt=Plot[v[t,1,1,2],{t,0,3},Axes->False,Frame->True,FrameLabel->{"t","v(t)"}];
Export["/home/student/courses/MATH528/vplt.png",vplt]
```

/home/student/courses/MATH528/vplt.png

In[3]:=

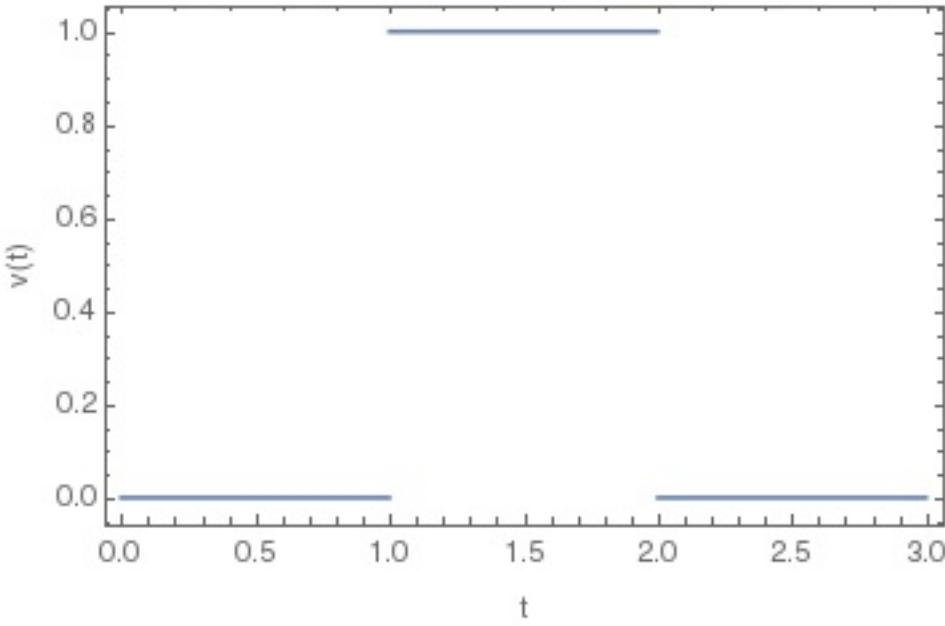


Figure 1. Single rectangular wave

2.1.1 $R - C$ (resistance-storage) circuit

- Model

$$Ry(t) + \frac{q(t)}{K} = Ry(t) + \frac{1}{K} \int_0^t y(\tau) d\tau = v(t) = V_0[u(t-a) - u(t-b)]$$

```
In[28]:= tmodel = R y[t] + 1/K Integrate[y[tau],{tau,0,t}] == v[t,V0,a,b]
```

$$\frac{\int_0^t y(\tau) d\tau}{K} + R y(t) = V_0(\theta(t-a) - \theta(t-b))$$

```
In[29]:=
```

- Laplace transform

$$RY(s) + \frac{Y(s)}{sK} = \frac{V_0}{s}[e^{-as} - e^{-bs}]$$

```
In[29]:= smodel = Simplify[LaplaceTransform[tmodel,t,s],a>0 && b>0] /.
LaplaceTransform[y[t], t, s] -> Y[s]
```

$$\frac{V_0(e^{-bs} - e^{-as}) + Y(s) \left(\frac{1}{K} + R s \right)}{s} = 0$$

```
In[30]:=
```

- Solution in frequency space

$$I(s) = \frac{V_0/R}{s + (RK)^{-1}} [e^{-as} - e^{-bs}] = F(s)[e^{-as} - e^{-bs}]$$

```
In[32]:= sol[s_]=Simplify[Y[s] /. Solve[smodel,Y[s]][[1,1]]]
```

$$\frac{K V_0 (e^{-as} - e^{-bs})}{K R s + 1}$$

```
In[33]:= InputForm[sol[s]]
```

$$((E^{-(a*s)} - E^{-(b*s)}) * K * V_0) / (1 + K * R * s)$$

```
In[34]:=
```

- Response function in time

$$f(t) = \mathcal{L}^{-1}(F)(t) = \frac{V_0}{R} e^{-t/(RC)}$$

In[34]:= F[s_]=(K*V0)/(1 + K*R*s)

$$\frac{KV_0}{KRs+1}$$

In[35]:= f[t_]:=InverseLaplaceTransform[F[s],s,t]

$$\frac{V_0 e^{-\frac{t}{KR}}}{R}$$

In[36]:=

- Response to single rectangular wave from frequency shifting

$$i(t) = f(t-a)u(t-a) - f(t-b)u(t-b)$$

In[42]:= y[t_,V0_,R_,K_,a_,b_] = f[t-a] UnitStep[t-a] - f[t-b] UnitStep[t-b]

$$\frac{V_0 \theta(t-a) e^{-\frac{t-a}{KR}}}{R} - \frac{V_0 \theta(t-b) e^{-\frac{t-b}{KR}}}{R}$$

In[43]:= yi[t_,V0_,R_,K_,a_,b_]:=InverseLaplaceTransform[sol[s],s,t]

$$\frac{V_0 e^{-\frac{t}{KR}} \left(\theta(t-a) e^{\frac{a}{KR}} - \theta(t-b) e^{\frac{b}{KR}} \right)}{R}$$

In[44]:= params = {V0->1,R->1,K->1,a->1,b->2};
solplt = Plot[{y[t,V0,R,K,a,b],yi[t,V0,R,K,a,b]} /. params,{t,0,4},Axes->False,
Frame->True,FrameLabel->{"t","v(t)"}];
Export["/home/student/courses/MATH528/solplt.png",solplt]

/home/student/courses/MATH528/solplt.png

In[45]:=

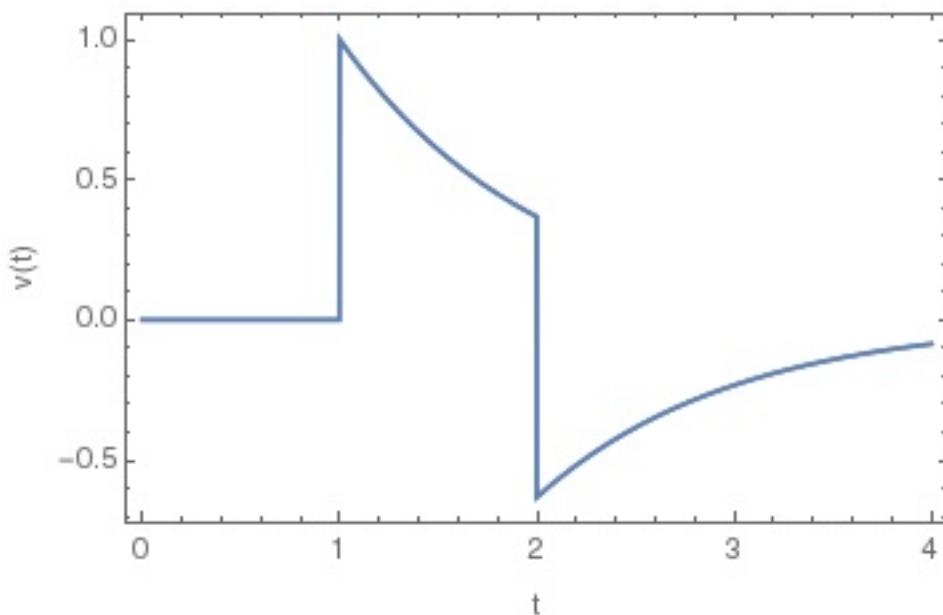


Figure 2. Circuit response to single rectangular wave